



---

### **Sheet (3): Digital Instruments**

- 1) Determine the maximum supply current required for a  $3\frac{1}{2}$ -digit LCD display that uses  $350\ \mu A$  per segment.
- 2) A  $4\frac{1}{2}$ -digit seven-segment LED display draws a maximum supply current of  $450\ mA$ . Calculate the current taken by each segment.
- 3) A frequency divider circuit is made up of a  $2\ MHz$  oscillator, a Mod- $2^4$  counter, and two decade counters. Determine the time period of the outputs from each counter.
- 4) Determine the quantization error for an ADC with a 16-bit output.
- 5) A 4-bit Flash ADC is designed with  $V_{ref} = 2V$ . Determine the thermometric code and the output digital code if the analog input is
  - a.  $100mV$
  - b.  $0.51V$
  - c.  $1.09V$
  - d.  $2.5V$
- 6) Design a Mod-12 counter using  $JK$  flip-flops.
- 7) Design a Mod-8 counter using  $D$  flip-flops.